

Worksheet - Series Circuit Problems, Episode 903 Name AK

Remember that in a series circuit:

- the current in every part of the circuit (is the same, adds up).
- the voltage supplied by the battery is the _____ voltage of the circuit, and the voltage drops across each resistor (is the same, adds up to) the total voltage.
- to calculate total resistance, (add, use reciprocals).

<p>$R_1 = 10\Omega$</p> <p>$R_2 = 20\Omega$</p> <p>$I_T = 3A$</p> <p>$R_T = \frac{30\Omega}{3A}$</p> <p>$I_1 = 3A$</p> <p>$I_2 = 3A$</p> <p>$V_1 = 30V$</p> <p>$V_2 = 60V$</p>	<p>$R_1 = 6\Omega$</p> <p>$R_2 = 14\Omega$</p> <p>$R_3 = 10\Omega$</p> <p>$I_T = 2A$</p> <p>$R_T = \frac{30\Omega}{2A}$</p> <p>$I_1 = 2A$</p> <p>$I_2 = 2A$</p> <p>$I_3 = 2A$</p> <p>$V_1 = 12V$</p> <p>$V_2 = 28V$</p> <p>$V_3 = 20V$</p>
<p>$R_1 = 10\Omega$</p> <p>$R_2 = 25V$</p> <p>$I_T = 5A$</p> <p>$V_1 = 50V$</p> <p>$R_2 = 5\Omega$</p>	<p>$R_1 = 5\Omega$</p> <p>$R_2 = 15\Omega$</p> <p>$I_T = 5A$</p> <p>$V_1 = 25V$</p> <p>$V_2 = 75V$</p> <p>$V_T = 100V$</p>
<p>$R_1 = 5\Omega$</p> <p>$R_2 = 3\Omega$</p> <p>$R_3 = 2\Omega$</p> <p>$I_T = 2A$</p> <p>$R_T = \frac{10\Omega}{2A}$</p> <p>$V_1 = 10V$</p> <p>$V_2 = 6V$</p> <p>$V_3 = 4V$</p>	<p>R_1</p> <p>R_2</p> <p>$R_3 = 10\Omega$</p> <p>$I_T = 2A$</p> <p>$I_3 = 2A$</p> <p>$I_1 = 2A$</p> <p>$R_1 = 5\Omega$</p> <p>$R_2 = 5\Omega$</p> <p>$V_1 = 10V$</p>