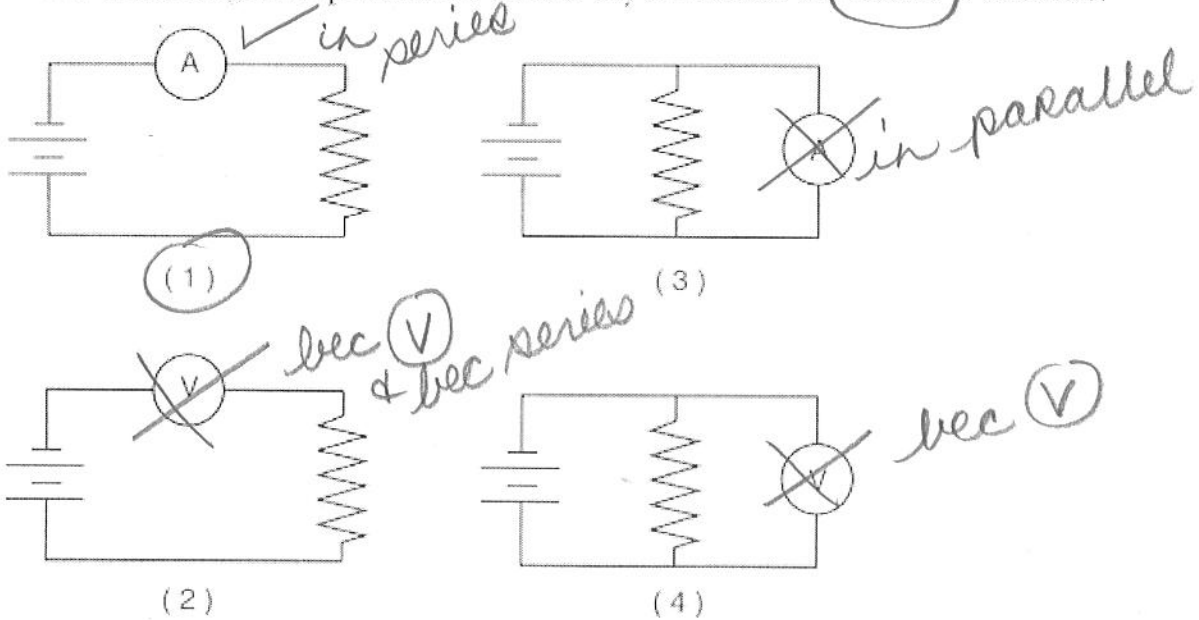


Series and Parallel Circuit Questions


1)

Which circuit diagram represents the correct way to measure the current in a resistor?



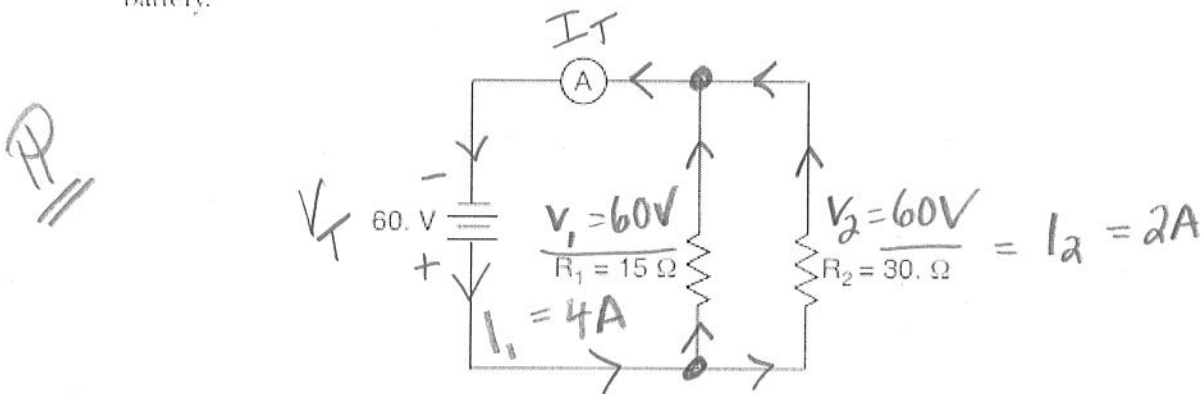2)

A 15-ohm resistor, 30-ohm resistor, and an ammeter are connected as shown with a 60-volt battery.



① Calculate the equivalent resistance of R_1 and R_2 . [Show all work, including the equation and substitution with units.] [2]

② Determine the current measured by the ammeter. [1]

X Calculate the rate at which the battery supplies energy to the circuit. [Show all work, including the equation and substitution with units.] [2]

③ If another resistor were added in parallel to the original circuit, what effect would this have on the current through resistor R_1 ? [1]





prove your answer
do the math
new $R_T = 5\Omega$ + new $I_T = 12A$

(1) adding a R in $\parallel \downarrow R_T \therefore \uparrow I_T$
(II) but V_T not changed so still 60V across each R so still 4A across R_1

3)

Which circuit has the largest equivalent resistance?

R_T

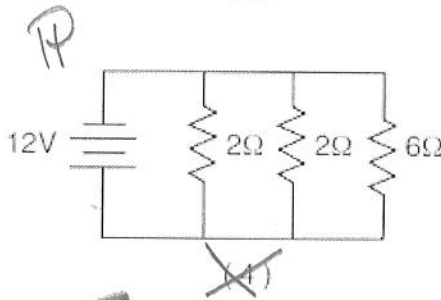
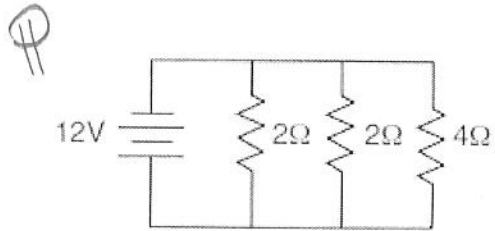
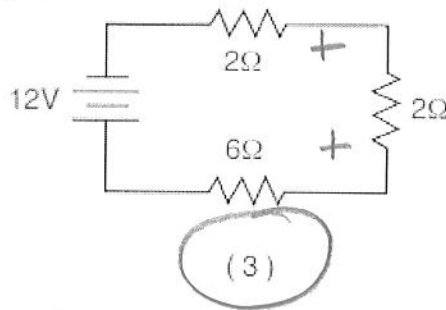
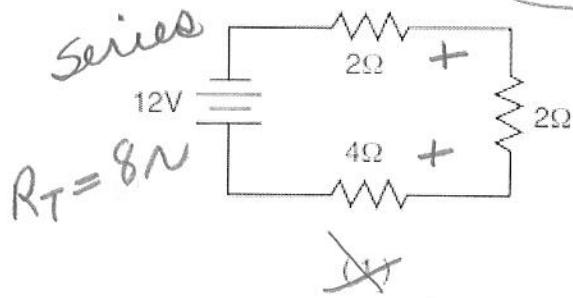


in Ⓟ $R_T < \text{smallest } R$
 $\therefore R_T < 2\Omega$

4)

Which circuit diagram represents voltmeter V connected correctly to measure the potential difference across resistor R_2 ?

$V_2 = ?$

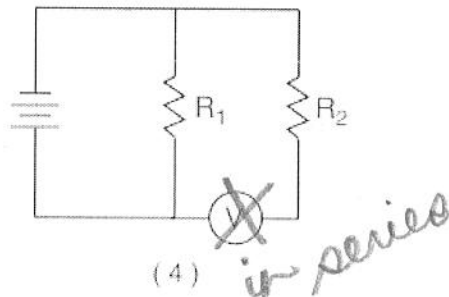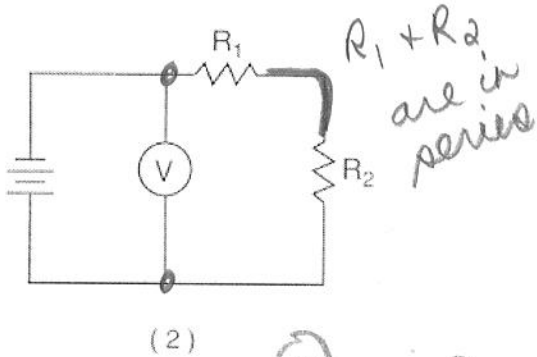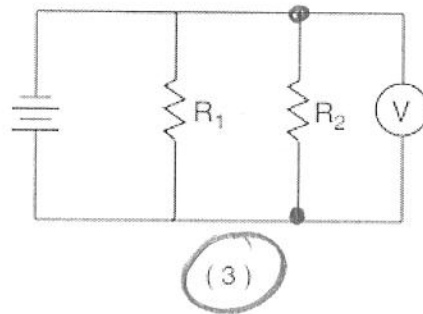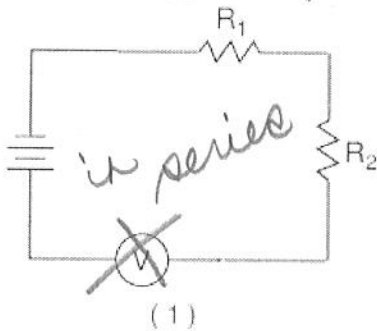

this V is reading total R across both R .

5)

Which combination of units can be used to express electrical energy? = J is the unit for E = start somewhere

~~(1) volt/coulomb~~

~~(2) coulomb/volt~~

(3) volt·coulomb

~~(4) volt·coulomb·second~~

* (iii) $V \cdot C = \frac{J}{C} \cdot C = J$

6)

A student constructed a series circuit consisting of a 12.0-volt battery, a 10.0-ohm lamp, and a resistor. The circuit does not contain a voltmeter or an ammeter. When the circuit is operating, the total current through the circuit is 0.50 ampere.

In the space in your answer booklet, draw a diagram of the series circuit constructed to operate the lamp, using symbols from the Reference Tables for Physical Setting/Physics. [1]

Determine the equivalent resistance of the circuit. [1]

$\frac{V_T = 12V}{I_T = 0.5A} = 24\Omega$


Determine the resistance of the resistor. [1]

14Ω

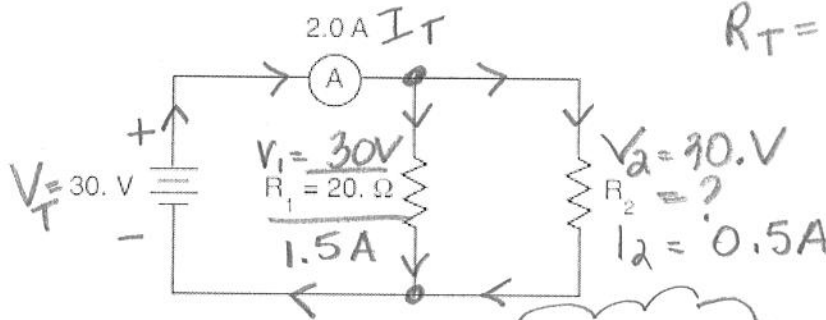7)

$R_T = R_1 + R_2 - R_2$
 $-R_2 = 24\Omega - 10\Omega = 14\Omega$

A 20.-ohm resistor, R_1 , and a resistor of unknown resistance, R_2 , are connected in parallel to a 30.-volt source, as shown in the circuit diagram below. An ammeter in the circuit reads 2.0 amperes.



$R_T = \frac{V_T}{I_T} = \frac{30.0V}{2.0A} = 15\Omega$

$\frac{V}{I} = \frac{VR}{I} = \frac{30.0}{0.5}$
 $R_2 = 60\Omega$

Determine the equivalent resistance of the circuit. [1]

$15\Omega = R_T$

Calculate the resistance of resistor R_2 . [Show all work, including the equation and substitution with units.] [2]


$R_2 = 60\Omega$

$(iv) J = Q \cdot V = J$
 $J = Q \cdot V = J$

8)





A 3-ohm resistor and a 6-ohm resistor are connected in parallel across a 9-volt battery. Which statement best compares the potential difference across each resistor?

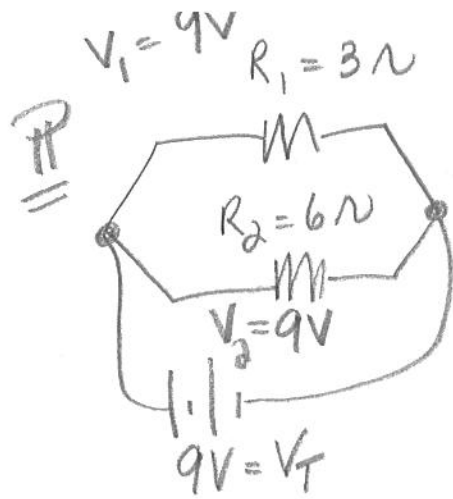- (1) The potential difference across the 6-ohm resistor is the same as the potential difference across the 3-ohm resistor. **T**
- (2) The potential difference across the 6-ohm resistor is twice as great as the potential difference across the 3-ohm resistor.
- (3) The potential difference across the 6-ohm resistor is half as great as the potential difference across the 3-ohm resistor.
- (4) The potential difference across the 6-ohm resistor is four times as great as the potential difference across the 3-ohm resistor.



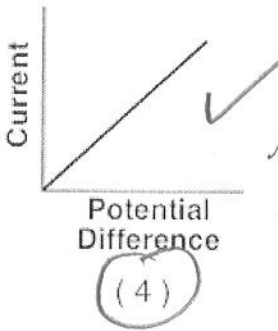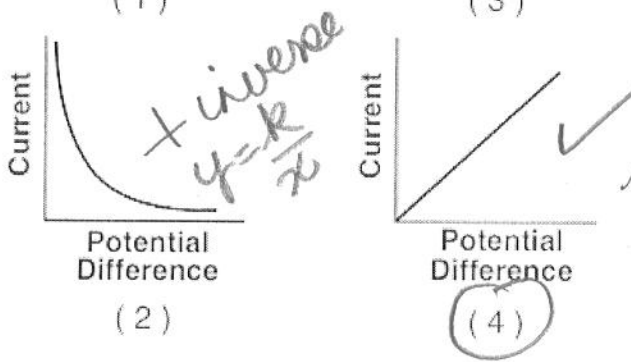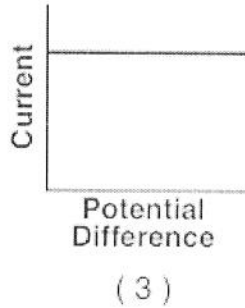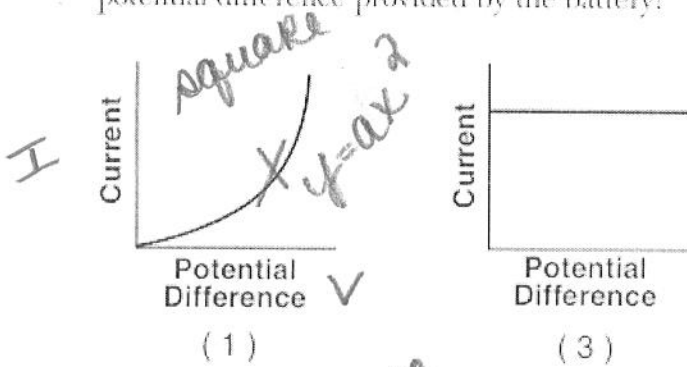9)

The resistance of a circuit remains constant. Which graph best represents the relationship between the current in the circuit and the potential difference provided by the battery?



Ohm's Law
 $V = IR$
 $\uparrow V = \uparrow I$ in a direct variation

this is the way we were supposed to graph it since voltage was the independent variable but then you don't get R as the slope (you get conductivity)

10)

An electric circuit consists of a variable resistor connected to a source of constant potential difference. If the resistance of the resistor is doubled, the current through the resistor is

- (1) halved
- (2) doubled
- (3) quartered
- (4) quadrupled

think dimmer switch

R + I are inversely related

$V_1 = 1, R_1$ $V_1 = 1V, I_1 = 1A, R_1 = 1\Omega$
 $1V = (1A)(1\Omega)$
 $1V = (?)(2\Omega)$ $V_2 = 1V, I_2 = ?, R_2 = 2\Omega$

11)

A 15-ohm resistor and a 20.-ohm resistor are connected in parallel with a 9.0-volt battery. A single ammeter is connected to measure the total current of the circuit.


In the space in your answer booklet, draw a diagram of this circuit using symbols from the Reference Tables for Physical Setting/Physics. [Assume the availability of any number of wires of negligible resistance.] [2]

Calculate the equivalent resistance of the circuit. [Show all work, including the equation and substitution with units.] [2]

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{15 \Omega} + \frac{1}{20 \Omega}$$

$$\frac{1}{R_T} = \frac{4}{60 \Omega} + \frac{3}{60 \Omega} = \frac{7}{60 \Omega}$$


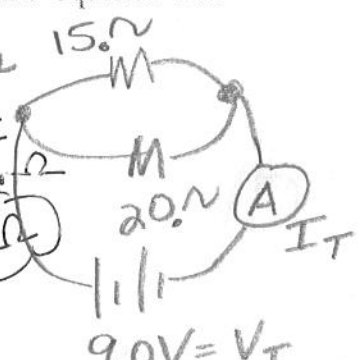
$$R_T = \frac{60 \Omega}{7} = 8.6 \Omega$$



12)

Circuit A has four 3.0-ohm resistors connected in series with a 24-volt battery, and circuit B has two 3.0-ohm resistors connected in series with a 24-volt battery. Compared to the total potential drop across circuit A, the total potential drop across circuit B is

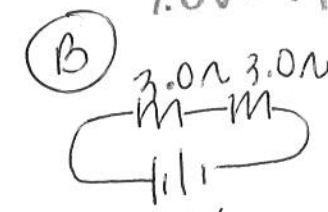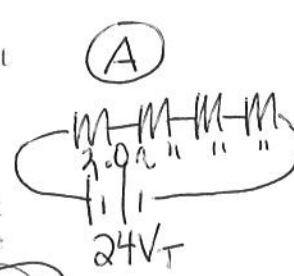
- (1) one-half as great (3) the same
 (2) twice as great (4) four times as great



potential drop =
 • same V but
 • diff R_T
 • diff I_T

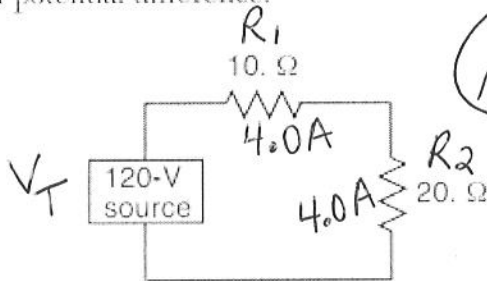13)

The diagram below represents a circuit consisting of two resistors connected to a source of potential difference.



series

What is the current through the 20.-ohm resistor?

- (1) 0.25 A (3) 12 A
 (2) 6.0 A (4) 4.0 A


$$R_T = R_1 + R_2 = 10 \Omega + 20 \Omega = 30 \Omega$$

$$\frac{V_T}{R_T} = \frac{I_T R_T}{R_T} = \frac{120 V}{30 \Omega} = I_T = 4.0 A$$

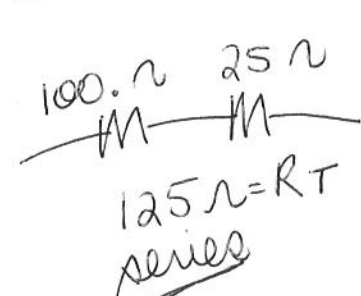14)

A simple circuit consists of a 100.-ohm resistor connected to a battery. A 25-ohm resistor is to be connected in the circuit. Determine the smallest equivalent resistance possible when both resistors are connected to the battery. [1]

put 25 ohm R into P for an R_T of 20 ohms





$$\frac{1}{R_T} = \frac{1}{100 \Omega} + \frac{1}{25 \Omega}$$

$$\frac{1}{R_T} = \frac{1}{100 \Omega} + \frac{4}{100 \Omega}$$


$$R_T = \frac{100 \Omega}{5} = 20 \Omega$$

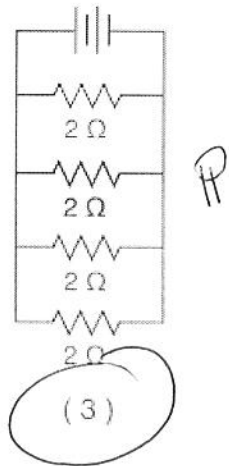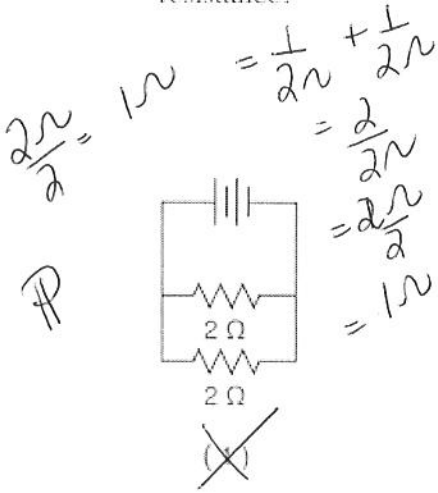15)


23 Which circuit has the smallest equivalent resistance?



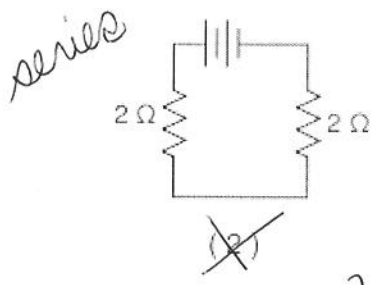$\frac{2\Omega}{4} = 0.5\Omega$
 $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$
 $\frac{1}{R_T} = \frac{1}{2\Omega} + \frac{1}{2\Omega} + \frac{1}{2\Omega} + \frac{1}{2\Omega} = \frac{4}{2\Omega}$
 $R_T = \frac{2\Omega}{4} = 0.5\Omega$



$R_T = 2\Omega + 2\Omega = 4\Omega$

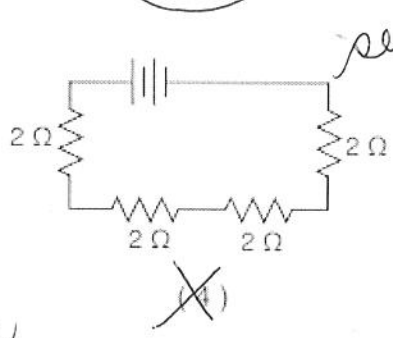

$R_T = 2\Omega \cdot 4 = 8\Omega$