

Circuit Pointers

1) watch placement of \textcircled{V} & \textcircled{A} !



2)



watch which voltage
or current is being
asked for!

V_1 or V_T I_2 or I_T
etc

3) I can be measured in mA but
to use equations must be in A!

$$24 \text{ mA} \times \frac{1 \text{ A}}{1000 \text{ mA}} = 0.024 \text{ A}$$

* learn your metric conversions *

4) Power is not Resistance

$$P = IV$$

$$W = AV$$

$$R = \frac{V}{I}$$

$$S = \frac{V}{A}$$

Ohm's Law Pointers

- 1) • graph V vs I for any resistor
 - title = V vs I for ...
 - $\phi V = \phi I \therefore (0,0)$ is always a data pt !
 - can graph using mA but when calculating slope must be in A.

$$1.3 \text{ mA} \times \frac{1 \text{ A}}{1000 \text{ mA}} = 0.0013 \text{ A}$$

- 2) • Slope of a V vs I graph NOT just
 - NOT slope of I vs V
 - NOT $\frac{\Delta I}{\Delta V}$!

$$R = \frac{V}{I}$$

$$\text{slope} = \frac{\Delta Y}{\Delta X} = \frac{\Delta V}{\Delta I} = \frac{V_2 - V_1}{I_2 - I_1} = \frac{V}{A} = R$$

* units everywhere

- Ohm's Law $V = IR$ • as voltage ↑
current ↑ in
a direct proportion